

Half-Subtractor :

A half Subtractor performs Subtraction of two -binary numbers (digits, bits).

→ It outputs the difference and the borrow that may occur during the subtraction process.

The half Subtractor takes two binary inputs.

A: Minuend (The number from which another number is subtracted).

B: Subtrahend (The number to be subtracted)

Outputs :

The half Subtractor produces two outputs

1. Difference (D): This represents the result of $A - B$

2. Borrow (B_0): This indicates whether a borrow was needed during the subtraction.

→ A borrow occurs when the minuend (A) is less than Subtrahend (B)

Truth-table :

A	B	Difference (D)	Borrow (B_0)
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

Boolean Expression:

$$D = A \oplus B$$

$$B_0 = \bar{A}B$$

Gate-level implementation:

